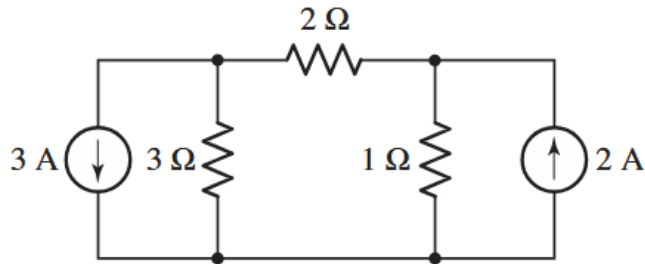



HW 3 - Zeshui Song

- 4.6 6. Calculate the power dissipated in the $1\ \Omega$ resistor of Fig. 4.36.




■ FIGURE 4.36

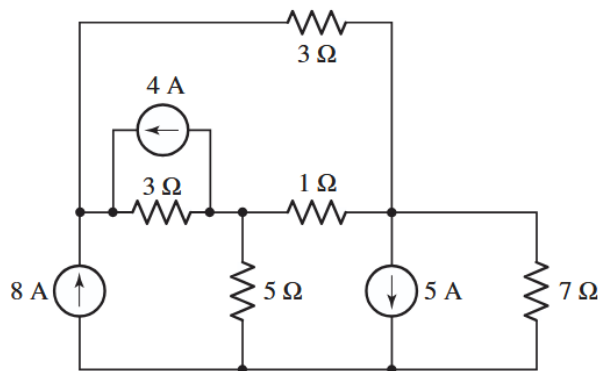- 4.12 12. Using the bottom node as reference, determine the voltage across the $5\ \Omega$ resistor in the circuit of Fig. 4.42, and calculate the power dissipated by the $7\ \Omega$ resistor.




■ FIGURE 4.42

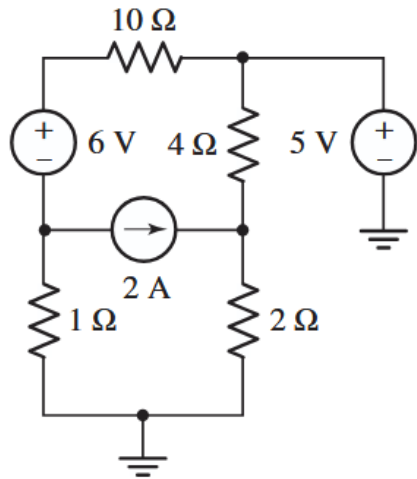- 4.20 20. For the circuit of Fig. 4.50, determine all four nodal voltages.




■ FIGURE 4.50

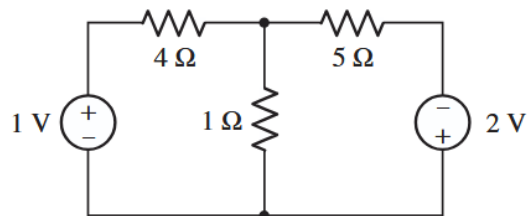- 4.32 32. Determine the currents flowing out of the positive terminal of each voltage source in the circuit of Fig. 4.60.




■ FIGURE 4.60

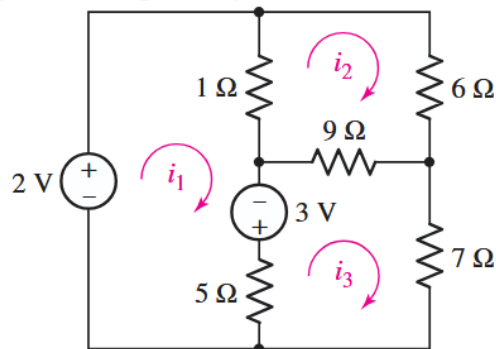- 4.36 36. Calculate the power dissipated by each resistor in the circuit of Fig. 4.63.




■ FIGURE 4.63

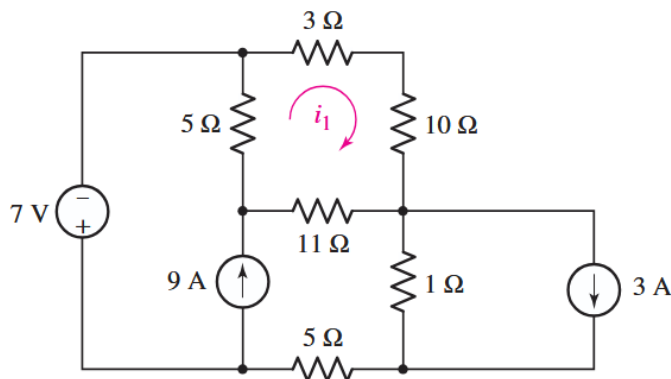- 4.46** 46. For the circuit of Fig. 4.73, determine the mesh current i_1 and the power dissipated by the $1\ \Omega$ resistor.




■ **FIGURE 4.73**

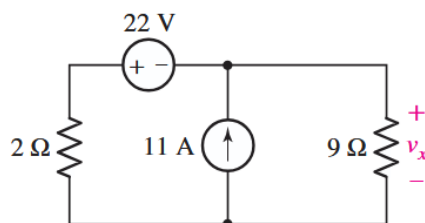- 4.56** 56. Solve for the voltage v_x as labeled in the circuit of Fig. 4.82 using (a) mesh analysis. (b) Repeat using nodal analysis. (c) Which approach was easier, and why?




■ **FIGURE 4.82**

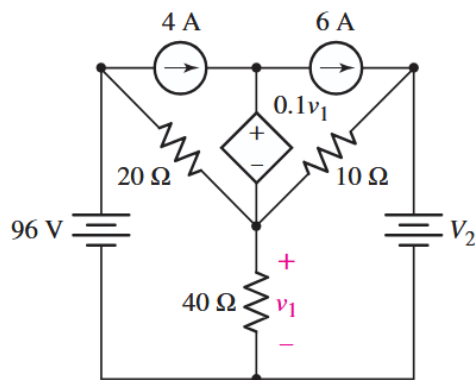- 4.57** 57. Consider the five-source circuit of Fig. 4.83. Determine the total number of simultaneous equations that must be solved in order to determine v_1 using (a) nodal analysis; (b) mesh analysis. (c) Which method is preferred, and does it depend on which side of the $40\ \Omega$ resistor is chosen as the reference node? Explain your answer.




■ **FIGURE 4.83**

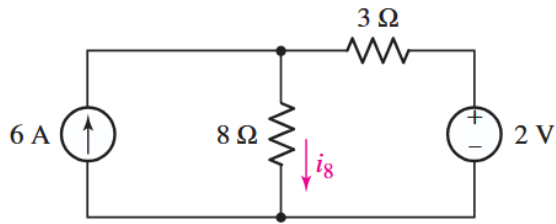- 5.3 3. Considering the circuit of Fig. 5.48, employ superposition to determine the two components of i_8 arising from the action of the two independent sources, respectively.




■ FIGURE 5.48

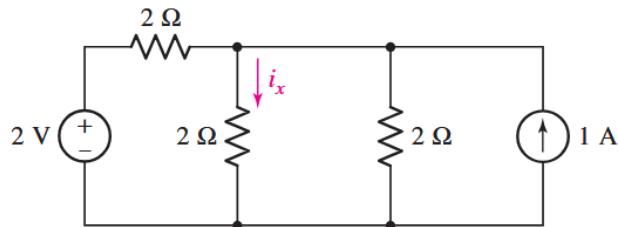- 5.5 5. (a) Using superposition to consider each source one at a time, compute i_x . (b) Determine the percentage of i_x arising from each source. (c) Adjusting only the current source, alter the circuit to double i_x .




■ FIGURE 5.50

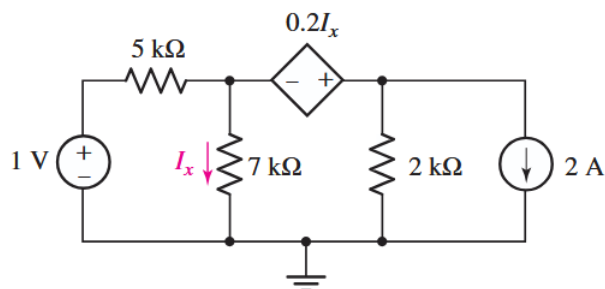- 5.11 11. Employ superposition principles to obtain a value for the current I_x as labeled in Fig. 5.56.



■ FIGURE 5.56

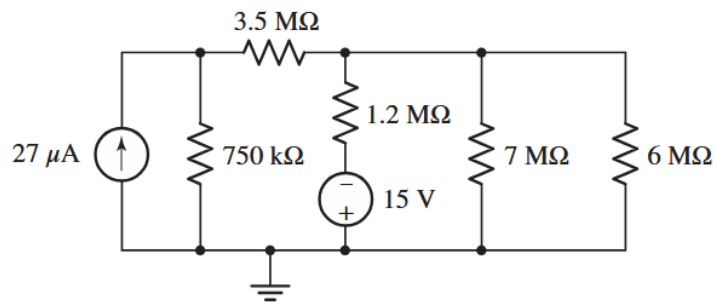- 5.18 18. (a) Using repeated source transformations, reduce the circuit of Fig. 5.62 to a voltage source in series with a resistor, both of which are in series with the $6\text{ M}\Omega$ resistor. (b) Calculate the power dissipated by the $6\text{ M}\Omega$ resistor using your simplified circuit.



■ FIGURE 5.62